

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 2, 2016/2017

EEE2146 – MICROELECTRONIC CIRCUIT ANALYSIS AND DESIGN

(All sections / Groups)


4 MARCH 2017
9.00 a.m – 11.00 a.m
(2 Hours)

INSTRUCTIONS TO STUDENTS

1. This examination paper consists of 6 pages with 4 questions only.
2. Attempt **ALL FOUR** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please print all your answers in the Answer Booklet provided.

Question 1

- (a) Compute the transistor base current, I_B , emitter current, I_E , emitter voltage, V_E and base voltage, V_B (with respect to ground) of the circuit shown in Figure Q1. Given that $V_{CC} = 9\text{ V}$ and the transistor $V_{BE(\text{active})} = 0.7\text{ V}$, current gain $\beta = 100$ and early voltage $V_A = \infty$. [7 marks]
- (b) Draw the small-signal equivalent circuit of the amplifier circuit in Figure Q1 using the simplified hybrid model. [5 marks]
- (c) From the small-signal equivalent circuit, determine the small signal input resistance, R_{IN} and the overall voltage gain, $\frac{V_o}{V_s}$. Given that voltage equivalence of temperature $V_T = 26\text{ mV}$. [13 marks]

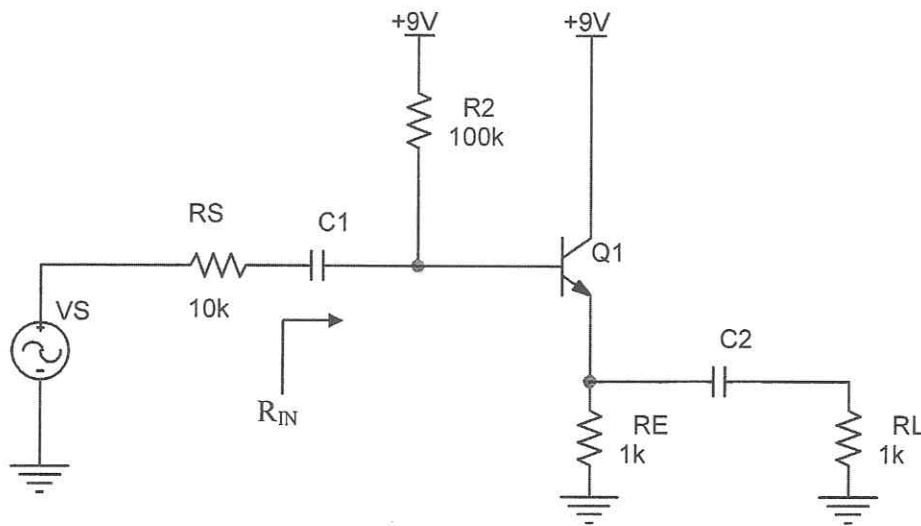**Figure Q1****Continued...**

Question 2

The circuit shown in Figure Q2 is a common-source amplifier. The transistor has $V_t = 1.5\text{V}$, $k'_n(W/L) = 0.25\text{ mA/V}^2$ and $V_A = 50\text{ V}$.

- (a) From the DC analysis, compute the values for DC drain current, I_D and DC drain voltage, V_D . Assume the DC gate current, $I_G = 0$. [7 marks]
- (b) Draw a small-signal equivalent circuit for the circuit shown in Figure Q2 using the simplified hybrid model. [5 marks]
- (c) Derive and compute the small-signal voltage gain, $\frac{v_o}{v_i}$, then compute the input resistance R_{IN} . [13 marks]

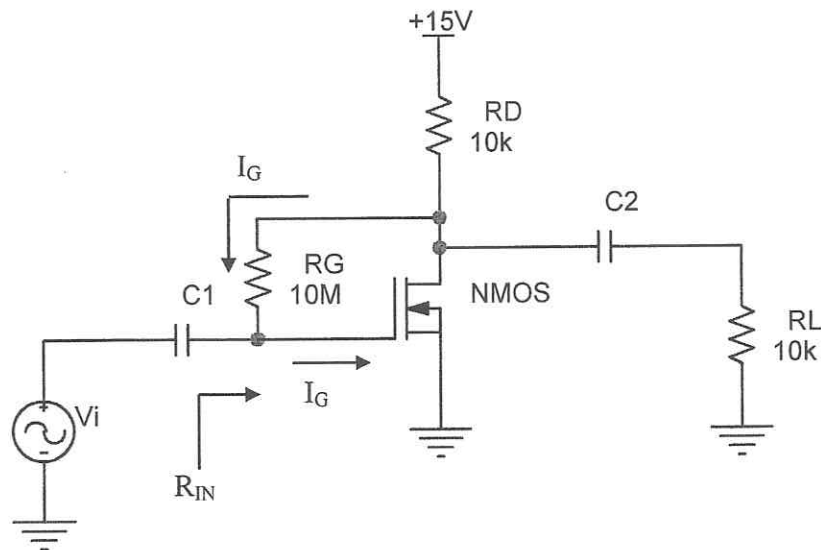


Figure Q2

Question 3

Figure Q3 below shows a MOSFET current mirror and a MOSFET differential amplifier. The voltage supply $V_{DD} = V_{SS} = 1.5V$. Assume that all transistors are identical (same k_n and V_t) and the transistors are in saturation.

- (a) Find I_{REF} if $V_{GS4} = V_{GS3} = 1V$ and $R_1 = 2.5k\Omega$. Then, compute I_q when $(W/L)_4 = 2$, $(W/L)_3 = 4$, $k_n = 200\mu A/V^2$ and $V_t = 0.5V$. [6 marks]

- (b) Draw the differential-mode small signal equivalent circuit for the differential amplifier below, then prove that the differential-mode voltage gain,

$$A_d = \frac{V_{od}}{V_{id}} = -g_m (R_D \parallel r_o). \quad [9 \text{ marks}]$$

- (c) Then, compute the values of R_{D1} and R_{D2} . Assume M1 and M2 are identical with $V_{OV} = 0.5$, early voltage, $V_A = \infty$ and the differential-mode voltage gain, $A_d = -250$. [10 marks]

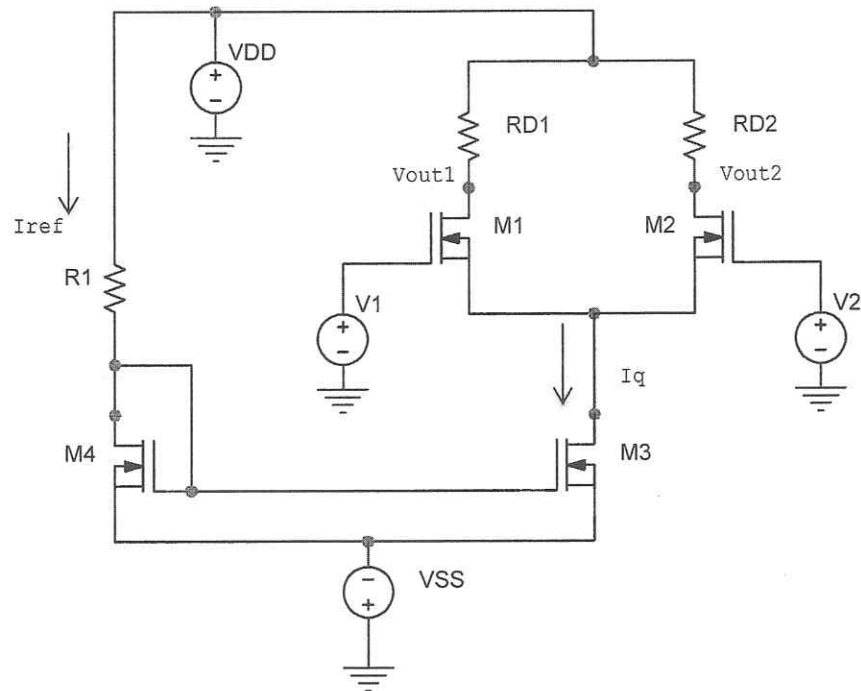
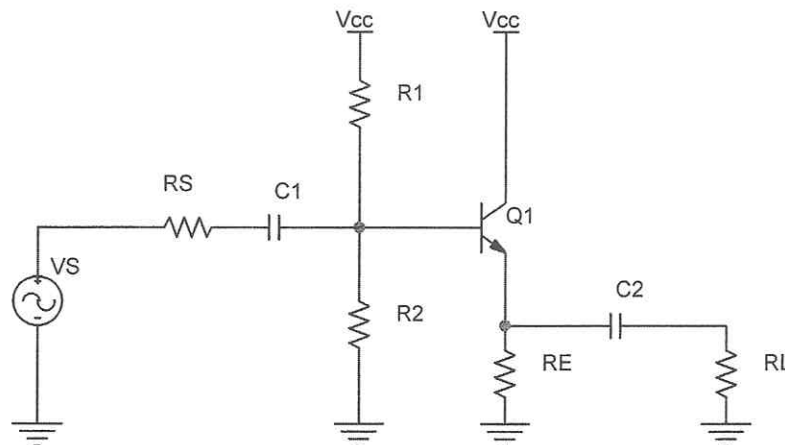


Figure Q3

Question 4


- (a) Draw a low frequency small signal equivalent circuit of the circuit shown in Figure Q4 (a) using hybrid- π model. Ignore the effect of the transistor output resistance, r_o . Then, derive the equations for the lower cutoff frequencies f_{C1} and f_{C2} of the circuits. Use necessary equivalent circuits to show in your derivations.

[11 marks]

**Figure Q4(a)**

- (b) The non-inverting amplifier shown in Figure Q4 (b) is a series-series feedback transconductance amplifier. Derive the equations for gain A_f , output resistance R_{of} and input resistance R_{if} . Draw the amplifier equivalent circuit to assist the derivations.

[14 marks]

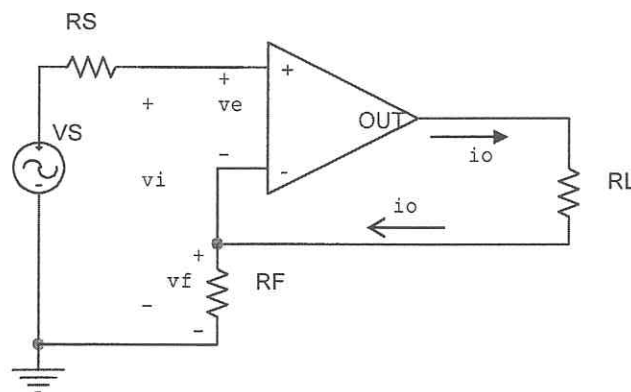**Figure Q4(b)**

Continued...

Appendix: Useful formula

$$V_T = \frac{kT}{q} \approx 26\text{mV}$$

$$I_B = \frac{I_C}{\beta_F}$$

$$I_E = \frac{-I_C}{\alpha_F}$$

$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$

$$C_b = \tau_F g_m$$

$$r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = \frac{V_T}{I_B}$$

$$g_m v_\pi = \beta i_b$$

$$r_o = \frac{1}{\frac{\partial I_C}{\partial V_{CE}}} = \frac{V_A}{I_C}$$

$$r_\mu = \beta r_o$$

$$V_{DS} < V_{GS} - V_t;$$

$$I_D = k' \left(\frac{W}{L} \right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$r_{ds} = \frac{V_{DS}}{i_D}$$

$$V_{DS} > V_{GS} - V_t;$$

$$I_D = \frac{k'}{2} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_{DS} > V_{DS(\text{SAT})};$$

$$I_D = \frac{k'}{2} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$V_A = V_M = L_{\text{eff}} \left(\frac{dX_d}{dV_{DS}} \right)^{-1} = \frac{1}{\lambda}$$

$$r_o = \frac{V_A}{I_D}$$

$$\phi_f = \frac{kT}{q} \ln \left(\frac{N_A}{n_i} \right)$$

$$\gamma = \frac{\sqrt{2q\epsilon N_A}}{C_{ox}}$$

$$V_t = V_{to} + \gamma \left(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$k' = \mu_n C_{ox}$$

$$V_{OV} = V_{GS} - V_t$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = k' \frac{W}{L} V_{OV} = \frac{2I_D}{V_{OV}}$$

$$C_{gs} = C_{gd} = \frac{C_{ox} WL}{2}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$\frac{\partial V_t}{\partial V_{BS}} = \frac{-\gamma}{2\sqrt{2\phi_f + V_{SB}}} = -\chi$$

$$\chi = \frac{C_{js}}{C_{ox}} = \frac{g_{mb}}{g_m}$$

$$f_T = \frac{1.5\mu_n}{2\pi L^2} V_{OV}$$

$$f_T = \frac{2\mu_n}{2\pi W_B^2} V_T$$

$$I_D = I_t \frac{W}{L} \exp\left(\frac{V_{OV}}{nV_T}\right) \left[1 - \exp\left(\frac{-V_{DS}}{V_T}\right) \right]$$

End of Paper